
 


# 1 Logic gates


## 1.1 AND

 


## 1.2 OR




## 1.3 NOT

 


## 1.4 NAND

 


## 1.5 NOR

 

## 1.6 XOR

 

## 1.7 XNOR

 


## 1.8 Basics

Nodes must have curly brackets at the end, even when empty. An optional anchor (#3) can be defined within round brackets to be addressed again later on.

```
\draw (x1,y1) to[<circuit element like , R,L,C>, i=<value>,v=<value>,l=<label>,color=<color>]
      (x2,y2) to[same as above]
      (x3,y3) to[same as above]
      ...
      (xn,yn);
```

## 1.9 Example 1

 

## 1.10 Example 2

Use `.in` and `.out` to refer to the inputs and outputs of gates.

